

Topic

Date

University of Delhi - Open Book Examination (Semester Examination)

NAME: Khushal Sachdeva

EXAMINATION ROLL NO.: 20003570032

COURSE NAME: (570) - (CBCS) B.Sc. (Hons.) Computer Science

SEMESTER: I

PAPER ID: 32341102

TITLE OF PAPER: Computer System Architecture

DATE: 20-03-2021

TIME: 9:30 am

NAME OF COLLEGE: (003) - Atma Ram Sanatan Dharam College

EMAIL ID: 88044@arsd.du.ac.in

MOBILE NO.: 8178594741

Topic

Date

QUESTION : 1

Ans.

a) $f(A, B, C, D) = \sum(1, 2, 3, 7, 8, 10)$
 $d(A, B, C, D) = \sum(0, 5, 6, 11, 15)$

AB \ CD	00	01	11	10
00	X	1 ₁	1 ₃	1 ₂
01		X ₄	1 ₇	X ₆
11			X ₁₅	
10	1 ₈		X ₉	1 ₁₀

I II

$$f = I + II$$

$$f = \overline{A}D + \overline{B}\overline{D} \quad (\text{Optimized expression})$$

b) $f = \overline{A}D + \overline{B}\overline{D}$
 using De-Morgan's law $[(X+Y)' = X'Y']$

$$f' = (\overline{A}D + \overline{B}\overline{D})' = (A + \overline{D})(B + \overline{D})$$

$$f = (A + \overline{D})(B + \overline{D})$$


c) $f = \overline{A}D + \overline{B}\overline{D} = \overline{A} \cdot 1 \cdot 1 \cdot D + 1 \cdot \overline{B} \cdot 1 \cdot \overline{D}$
 $= (\overline{A})(B + \overline{B})(C + \overline{C})(D) + (A + \overline{A})(\overline{B})(C + \overline{C})(\overline{D})$
 $= (\overline{A}B + \overline{A}\overline{B})(CD + \overline{C}D) + (A\overline{B} + \overline{A}\overline{B})(C\overline{D} + \overline{C}\overline{D})$
 $f = \overline{A}BCD + \overline{A}B\overline{C}D + \overline{A}\overline{B}CD + \overline{A}\overline{B}\overline{C}D$
 $+ A\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D}$

(Original expression)

Topic

Date

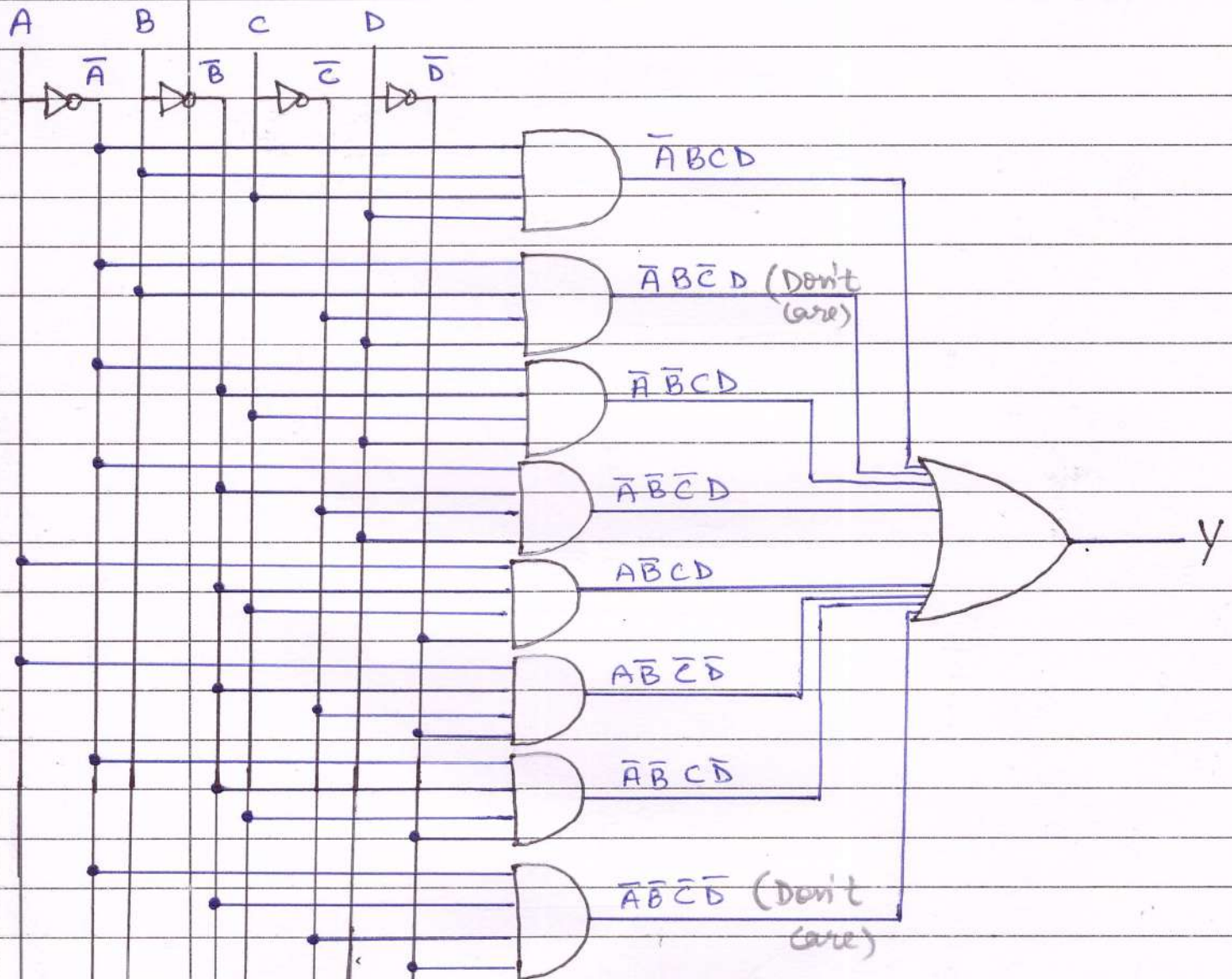c) $f = \bar{A}D + \bar{B}\bar{D}$ (Optimized form)
 $f = \bar{A}BCD + \bar{A}B\bar{C}D + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + A\bar{B}CD$
 $+ A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D}$ (original form)




Total No. of gates = 11
 in original expression

PAGE No - 2

Topic

Date

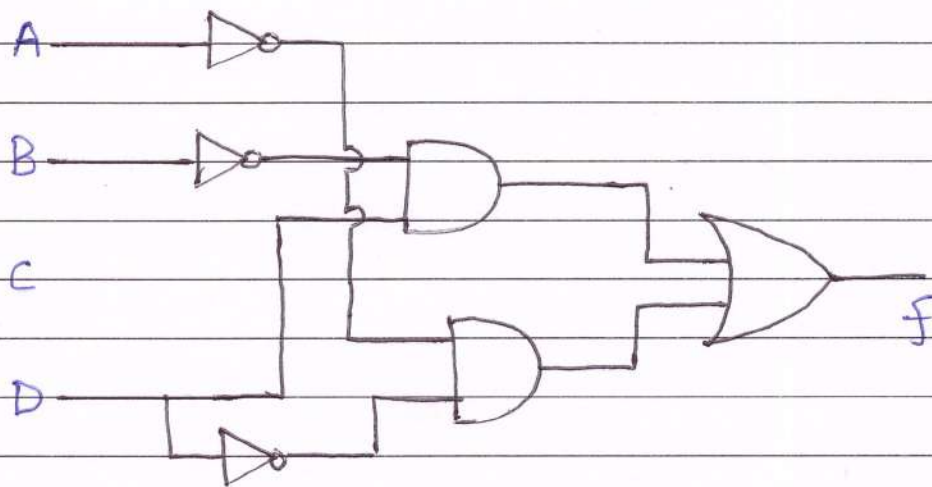

Total No. of gates = 6
in optimised form

d)

$$f = \bar{A}D + \bar{B}\bar{D}$$

$$f' = AB + AD + B\bar{D}$$

$$= AD + B\bar{D} + AB(D + \bar{D})$$

$$= AD + B\bar{D} + ABD + AB\bar{D}$$

$$= AD + ABD + B\bar{D} + AB\bar{D}$$

$$= AD(1 + B) + B\bar{D}(1 + A)$$

$$= AD(1) + B\bar{D}(1)$$

$$[1 + X = 1]$$

$$f' = AD + B\bar{D}$$

$$\bullet f \cdot f' = (\bar{A}D + \bar{B}\bar{D})(AD + B\bar{D})$$

$$= \bar{A}ADD + \bar{A}B\bar{D}\bar{D} + A\bar{B}D\bar{D} + B\bar{B}\bar{D}\bar{D}$$

$$= 0 + 0 + 0 + 0$$

$$= 0$$

$$\bullet f + f' = \bar{A}D + \bar{B}\bar{D} + AD + B\bar{D}$$

$$= \bar{A}D + AD + \bar{B}\bar{D} + B\bar{D}$$

$$= D(A + \bar{A}) + \bar{D}(B + \bar{B})$$

$$= D(1) + \bar{D}(1)$$

$$= D + \bar{D}$$

$$= 1$$

Topic

Date

$$\begin{aligned} e) \quad & AB + A(CD + C\bar{D}) \\ &= AB + AC(D + \bar{D}) \\ &= AB + AC(1) \\ &= A(B + C) \end{aligned}$$